

# Title Here

Oskar Weigl - ow610  
and  
Ryan Savitski - rs510

March 15, 2013

## Abstract

Write the abstract here

## Contents

<b>1</b>	<b>Notch Filter</b>	<b>2</b>
1.1	Filter Design . . . . .	2
1.2	Filter Topology . . . . .	2
1.3	Quantization . . . . .	3
1.4	Architecture . . . . .	3

# 1 Notch Filter

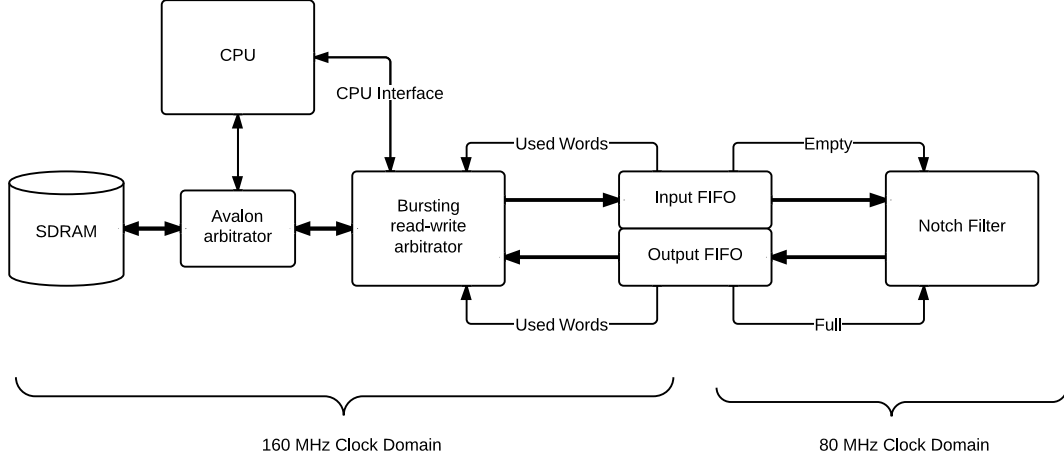


Figure 1: Block diagram of the Notch Filter hardware. FIFO buffers are used to allow efficient interleaved reads and writes to SDRAM. The buffers also serve as Clock Domain Crossing interfaces.

The Notch Filter module is a memory mapped hardware accelerator for the purpose of filtering a 16 bit signed input. It is a 2nd order notch filter tuned to to remove any spectral components at 1 kHz. The module is capable of Direct Memory Access, and includes optimisations for efficient access to the SDRAM, and uses a buffering, and Clock Domain Crossing strategy, to maximise performance.

## 1.1 Filter Design

The chosen filter type is a 2nd order notch filter. This filter order is the minimum required to generate the complex pole and zero pairs required to implement a notch filter. In fact, no higher order is needed, as the noise is a pure sinusoid, so the width of the stop-band can be very small, and as such, there are no additional zeroes required.

The filter is designed by simply placing a complex zero pair on the unit circle corresponding to the 1 KHz null we wish to create. To cancel the effect of this zero for other frequencies, we place a pole very close to it on the inside of the unit circle. The bandwidth of the filter is tuned by moving the complex pole radially.

In our case, we elect to place the pole such that the bandwidth of rejection is about 25Hz. This is was chosen as a good trade-off for several reasons. Firstly, placing the pole at this location makes the filter robust to coefficient quantisation, as discussed in Section 1.3. More importantly, this bandwidth is narrow enough to not affect the music, but wide enough to quickly suppress the overlaid sinusoid at the beginning of the sample. The magnitude of the resulting filter can be seen in Figure 2.

## 1.2 Filter Topology

Several different types of filter topologies were considered. It is clear that as a 2nd order

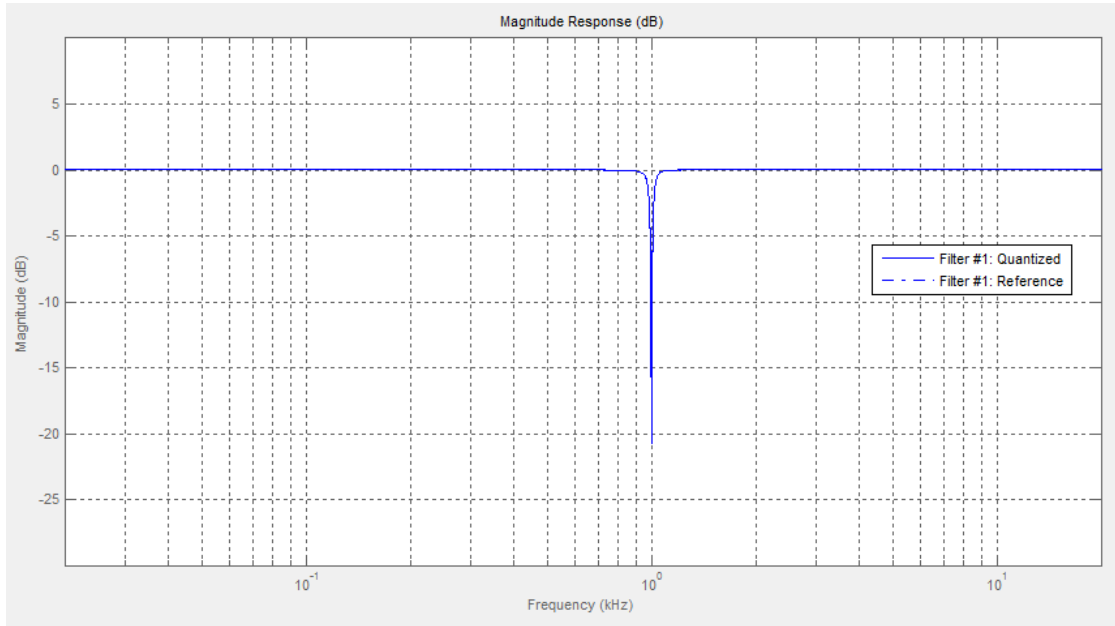


Figure 2: Magnitude response of both the full (double) precision and the quantised filter. The gain is negative infinity dB at 1 kHz.

The effects of quantization depends entirely on the chosen filter topology.

### 1.3 Quantization

### 1.4 Architecture

Assesment of speed (critical path) of different filter stuctures Describe diagram 1, (SDRAM slow, but good for sequential, interleaving)

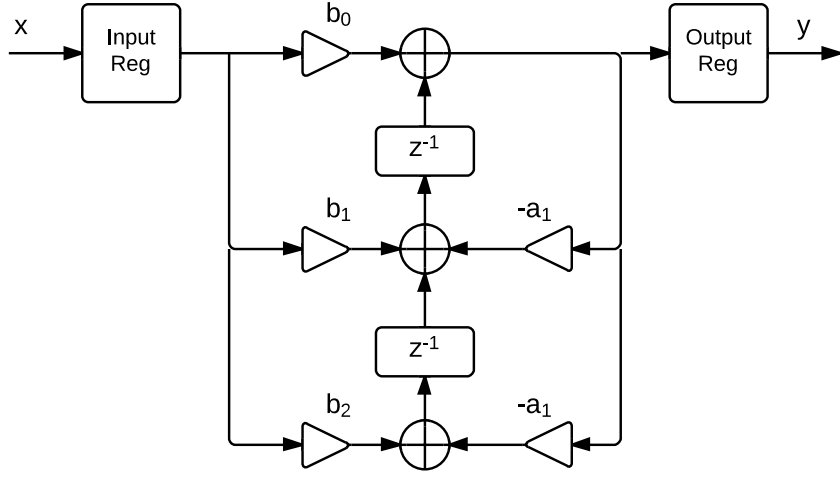


Figure 3: Second order Direct Form II Transposed filter architecture

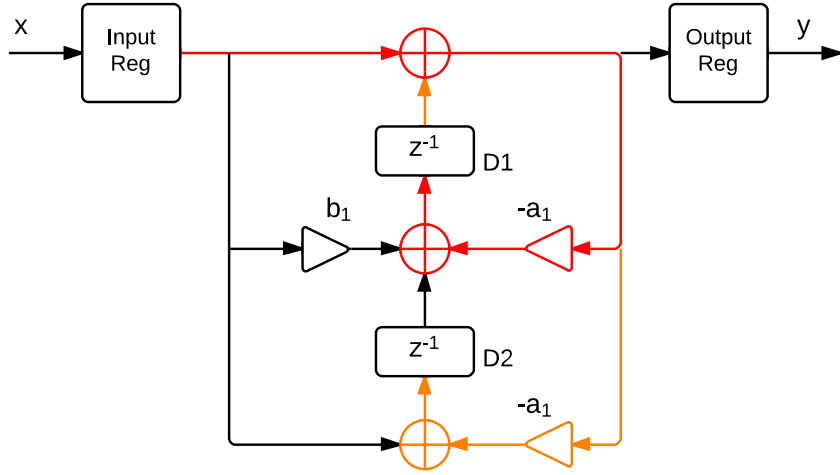


Figure 4: Annotated version of Figure 3, showing the main critical paths in the filter core. Shown in red is the path from the input register to the delay register D1. Shown in orange are the alternative paths that have almost as little slack as the red path.